

# Transconductance Amplifier

Shreshta Thumati\*

1. For a feedback transconductance amplifier in Fig 1.1, derive an approximate expression for the closed loop transconductance  $T$  for the case of  $GH \gg 1$ . Hence select a value of  $R_2$  to obtain  $T=100 \text{ mA/V}$ . If  $Q$  is biased to obtain  $g_m = 1 \text{ mA/V}$ , specify the value of the gain  $\mu$  of the differential amplifier to obtain an amount of feedback of 60 dB. If  $Q$  has  $r_o = 50 \text{ k}\Omega$  find the  $R_{out}$ .

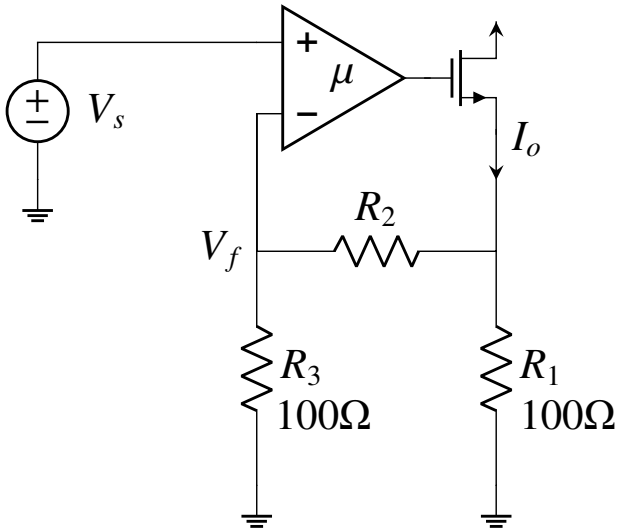


Fig. 1.1: Complete Circuit

**Solution:**

$$H = \frac{V_f}{I_o} \quad (1.1)$$

From Fig.1.2

$$V_x = ((R_2 + R_3) \parallel R_1) I_o \quad (1.2)$$

$$V_f = I_f R_3 \quad (1.3)$$

$$V_x - V_f = R_2 I_f \quad (1.4)$$

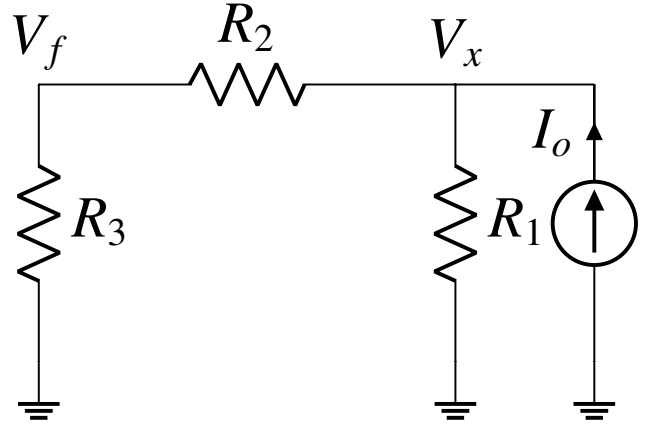


Fig. 1.2: Feedback Circuit

From equations 1.1 to 1.4 we get

$$H = \frac{V_f}{I_o} = \frac{R_1 R_3}{R_1 + R_2 + R_3} \quad (1.5)$$

As  $GH \gg 1$ ,

$$T = \frac{1}{H} \quad (1.6)$$

For  $T = 100 \text{ mA/V}$ ,

$$R_2 = 800 \Omega \quad (1.7)$$

$$\Rightarrow H = 10$$

$$G = \frac{I_o}{V_i} \quad (1.8)$$

From Fig. 1.3 we can see that

$$V_{gs} = \mu V_i - V_x \quad (1.9)$$

$$g_m V_{gs} - \frac{V_x}{r_o} = I_o \quad (1.10)$$

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.

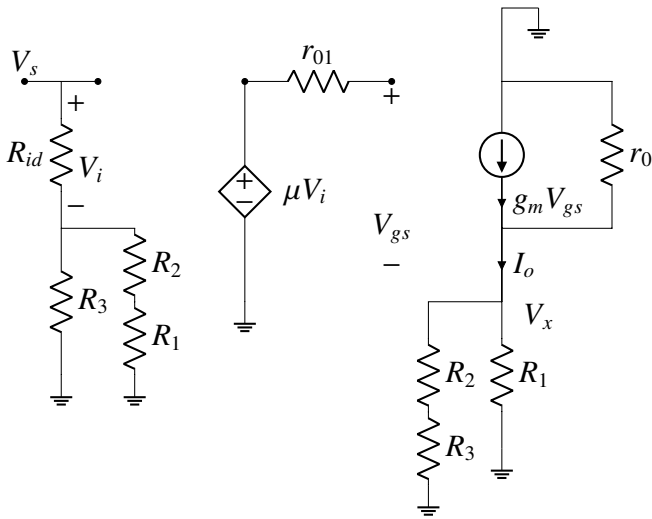


Fig. 1.3: Small signal model

From equations 1.9 to 1.10

$$G = \frac{I_o}{V_i} = \frac{g_m \mu r_o}{r_o + (1 + g_m r_o)((R_2 + R_3) \parallel R_1)} \quad (1.11)$$

Given  $GH = 60\text{dB}$ ,

$$20 \log_{10} GH = 60\text{dB} \quad (1.12)$$

$$\Rightarrow G = 100 \quad (1.13)$$

Substituting the values in the Eq. 1.11

$$\mu = 109180 \quad (1.14)$$

For output reistance,

$$R_o = r_o + g_m r_o((R_2 + R_3) \parallel R_1) + ((R_2 + R_3) \parallel R_1) \quad (1.15)$$

Substituting the values in Eq.1.15

$$R_o = 54.59\text{k}\Omega \quad (1.16)$$

$$R_{out} = R_o(1 + GH) \quad (1.17)$$

$$\Rightarrow R_{out} = 54.64\text{ M}\Omega$$

The following code generates the values

```
codes/ee18btech11041.py
```

The following code generates results from spice solution

```
codes/spice/ee18btech11041_spice.py
```

Parameter	Value
$G$	$100\text{A/V}$
$H$	$10\text{V/A}$
$GH$	$1000$
$T$	$0.1\text{A/V}$
$R_o$	$54.59\text{k}\Omega$
$R_{out}$	$54.64\text{M}\Omega$

TABLE 1

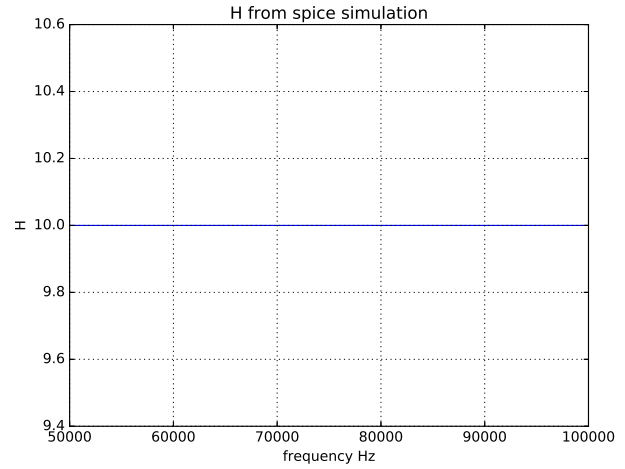


Fig. 1.4

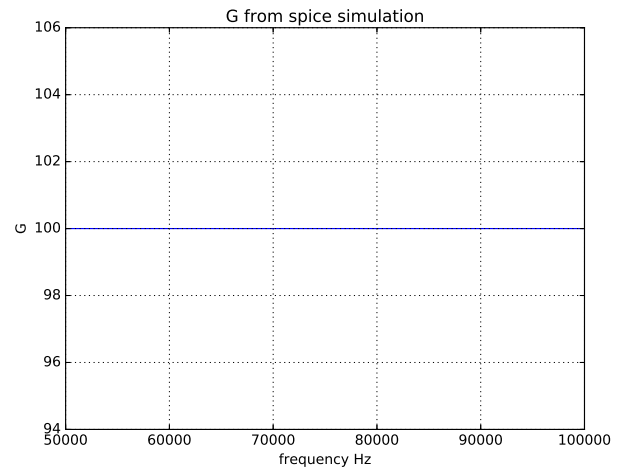


Fig. 1.5

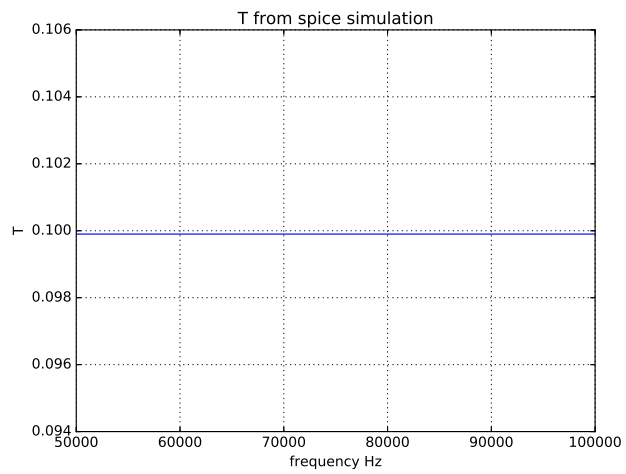


Fig. 1.6